

System Overview:

✓ Objective


- Provide **affordable**, **scalable**, and **reliable** power to off-grid communities, addressing the energy needs of households and small businesses.

✓ System


- Flexibility for AC & DC loads for Tier 1-4 Access
- AC Port: 240V, 1kW
- DC Port: 12V, 100W
- USBA/C Ports for low-power appliances
 - Overnight backup enabled by 3.7V Li-ion cell batteries.

✓ Power Sources

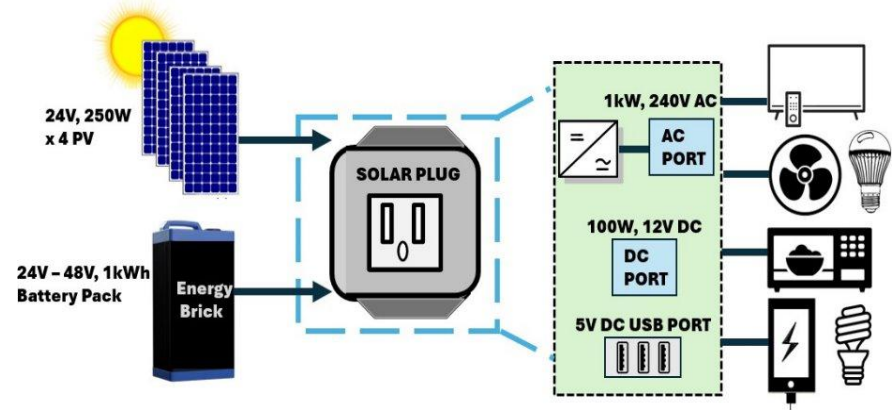- Multipoint operability directly from PV panels or battery pack




System block diagram of the Solar Plug

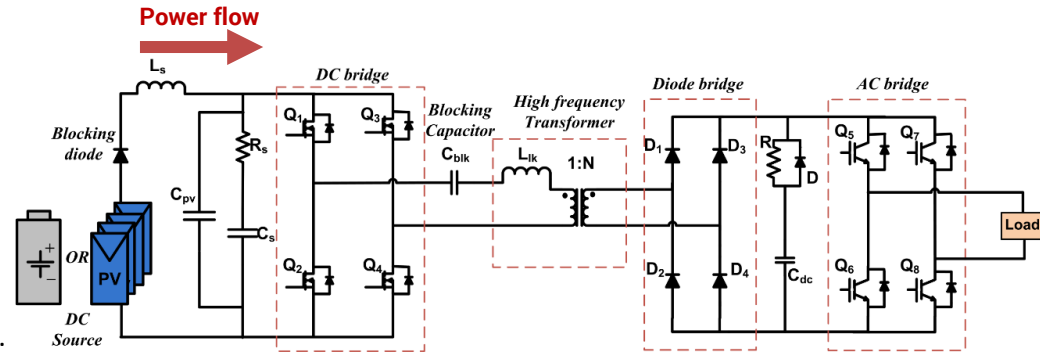

Circuit diagram of the proposed converter

Operating Principle – Overview

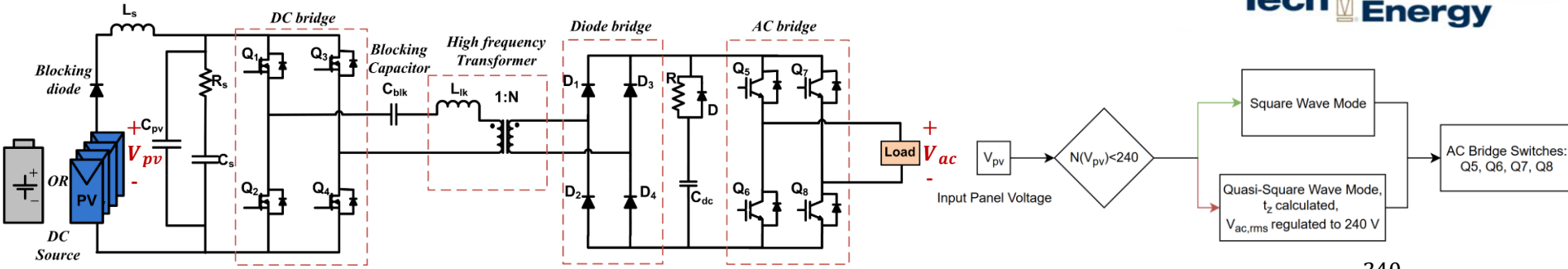

✓ DC-DC Stage

- DC Bridge switches at f_{sw} with 50% duty cycle
- Transformer (1:N) steps voltage up: NV_{pv}
- Diode Bridge rectifies voltage across C_{dc}

✓ DC-AC Stage

- **Square Wave Mode:** AC Bridge switches at f_o with 50% duty cycle (when $V_{pv} < \frac{240}{N}$)
- **Quasi-Square Wave Mode:** AC Bridge introduces **Dwell Time** to regulate RMS voltage to 240V (when $V_{pv} > \frac{240}{N}$)

Dwell Time, t_z when $V_{pv} > \frac{240}{N}$

$$t_z = \frac{t_o}{2} \times \left(1 - \frac{240^2}{(NV_{pv})^2} \right)$$

t_o : AC Voltage time period; $\left(\frac{1}{f_o} \right)$ where $f_o = 50/60\text{Hz}$


N : Transformer Turns Ratio

V_{pv} : Panel Voltage


V_{pv}	Mode	Dwell time t_z	Positive State		Negative State		Zero State	
			ON	OFF	ON	OFF	ON	OFF
$< \frac{240}{N}$	Square Wave	0	Q_5, Q_8	Q_6, Q_7	Q_6, Q_7	Q_5, Q_8	–	–
$> \frac{240}{N}$	Quasi-Square Wave	$\frac{t_o}{2} \left(1 - \frac{240^2}{(NV_{pv})^2} \right)$	Q_5, Q_8	Q_6, Q_7	Q_6, Q_7	Q_5, Q_8	Q_5, Q_7 after Negative State	$Q_1, Q_2, Q_3, Q_4, Q_6, Q_8$
							Q_6, Q_8 after Positive State	$Q_1, Q_2, Q_3, Q_4, Q_5, Q_7$

Table. Summary of Switching


Operating Principle – Simulated Results

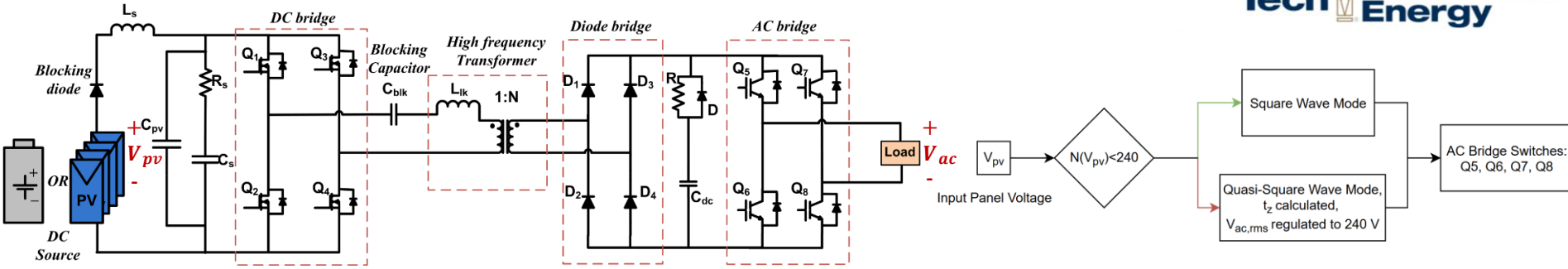

Square-Wave Mode

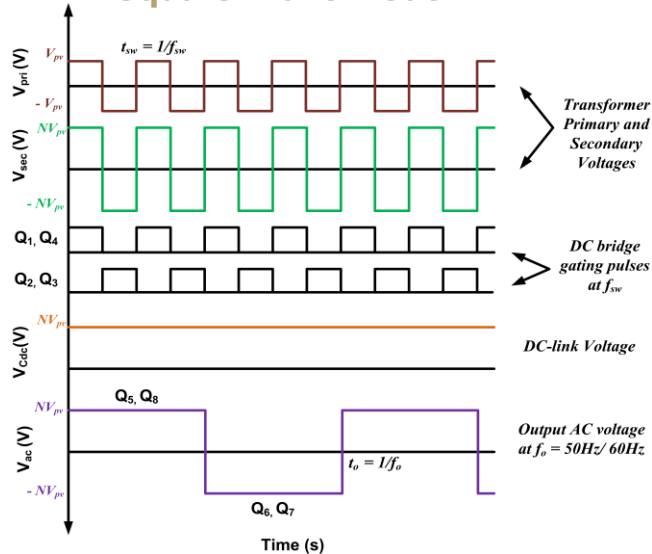


Quasi-Square Wave Mode

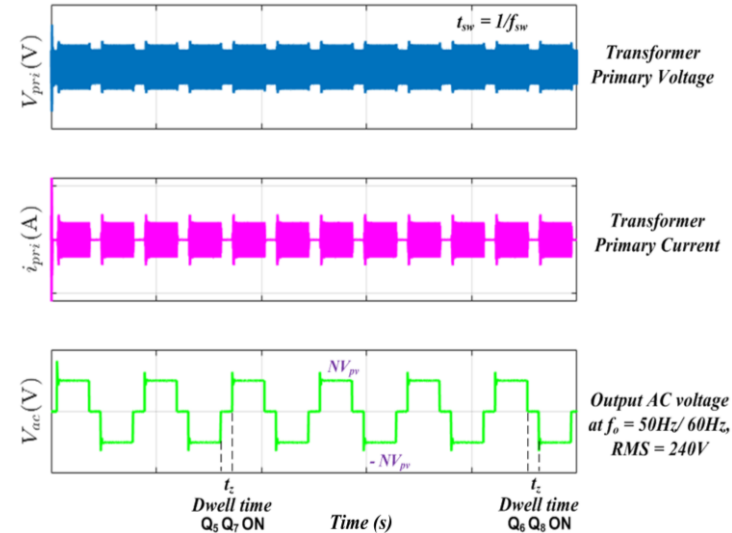

Simulation Results – Irradiance Step

✓ Transient Behavior

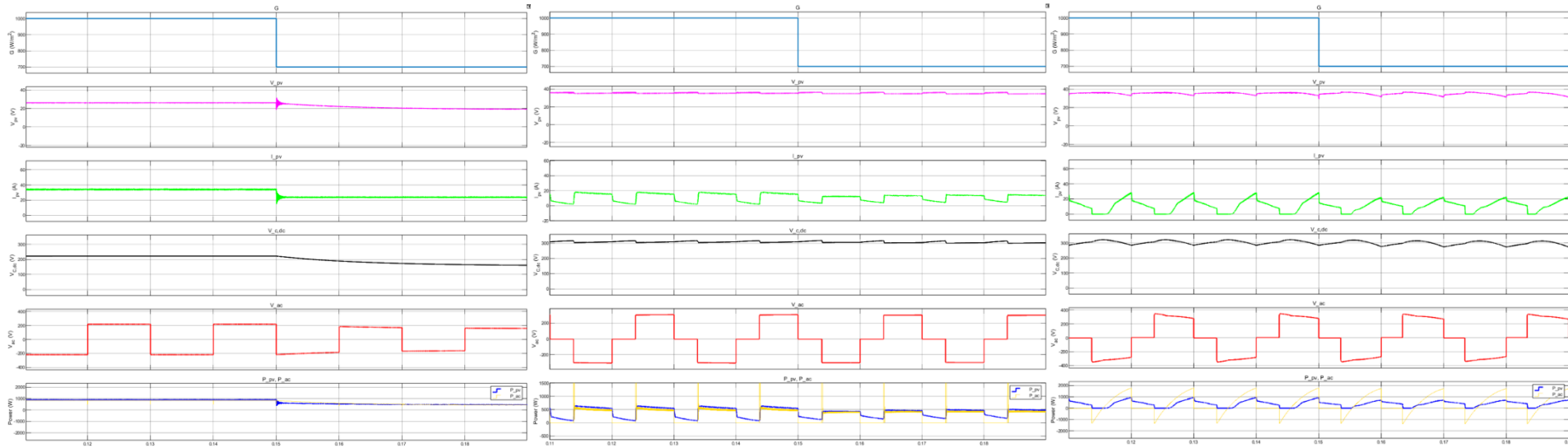- Irradiance Step: $G = 1000 \text{ W/m}^2 \rightarrow G = 700 \text{ W/m}^2$
- Converter output is stable under transient irradiance conditions



Resistive (57.6Ω) Load $\approx 1 \text{ kW}$

Rectified RC (250Ω, 470μF) Load

0.3pF RL (20Ω, 68mH) Load

Hardware Prototype – Overview & Parameters



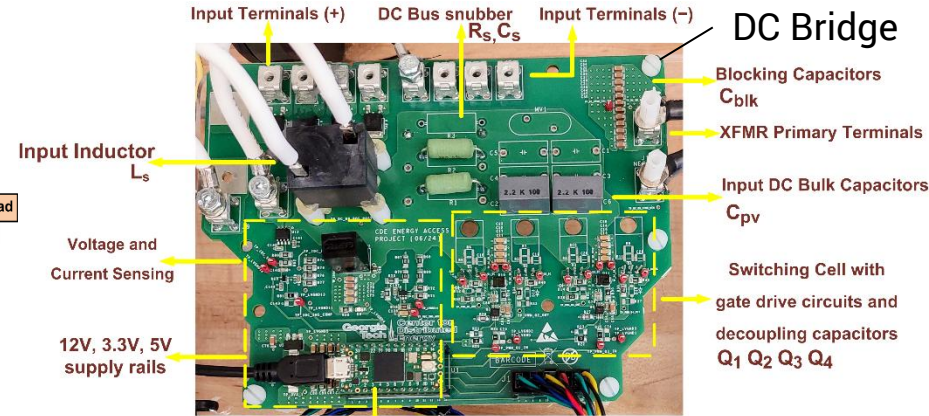
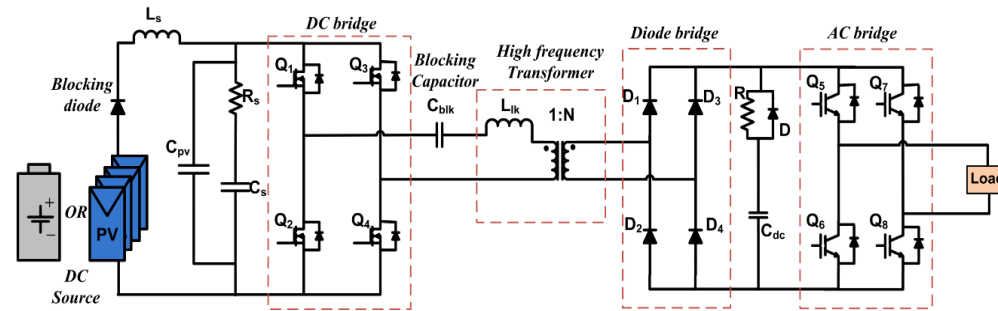


Table. Hardware prototype system parameters.

Param.	Value	Param.	Value	Param.	Value
f_{sw}	20kHz	P_{rated}	1kW	MOSFET , $R_{ds,on}$	1.7 mΩ
f_o	50/60Hz	Diode V_{fwd}	1.38V	IGBT $V_{ce,sat}$	1.5V
XFMR		L_s	10 uH		
L_m	900 uH	C_{pv}	4.4 uF		
N	10	R_s	0.5 Ω		
L_{lk}	150 nH	C_{dc}	10 uF		

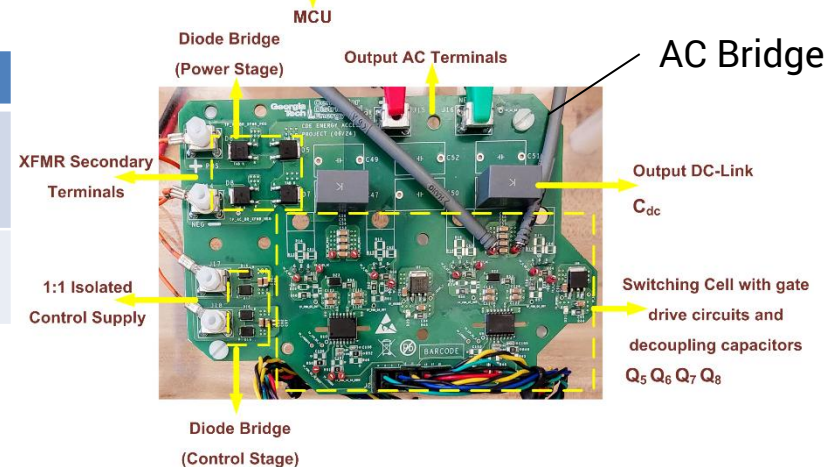


Hardware Validation – Resistive Load

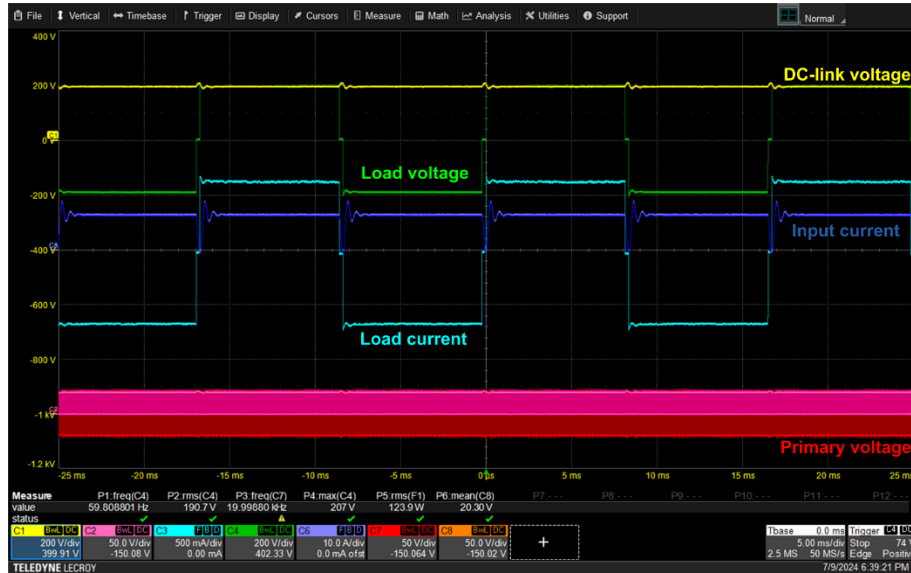

$V_{in} = 20V$

Load Parameters

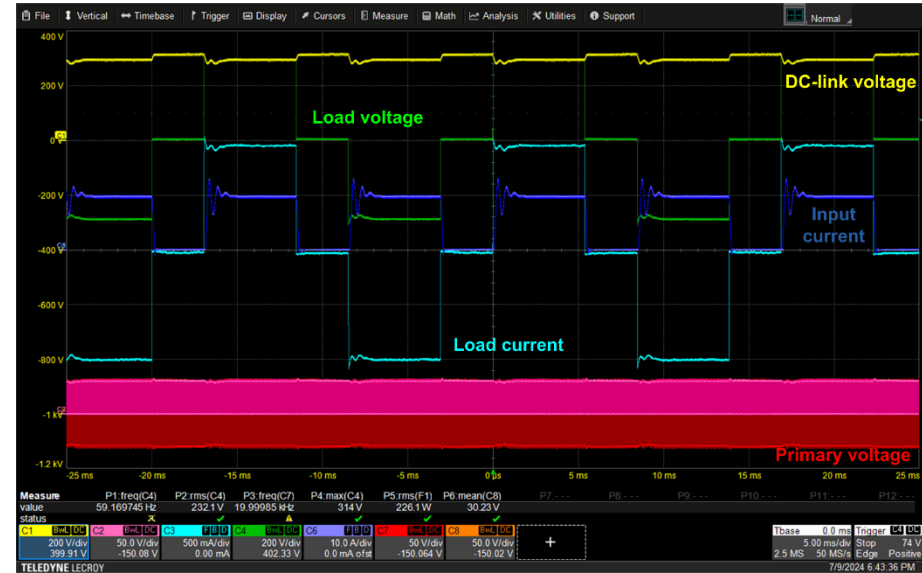- $P_{peak} \approx 190 \text{ W} @ 240V \text{ RMS}$
- $R_{load} = 302\Omega$



$V_{in} = 30V$

- Load Voltage
- Load Current
- DC-Link Voltage
- Input Current
- Primary Voltage


Hardware Validation – Electronic Load



$$V_{in} = 25V$$

Load Parameters

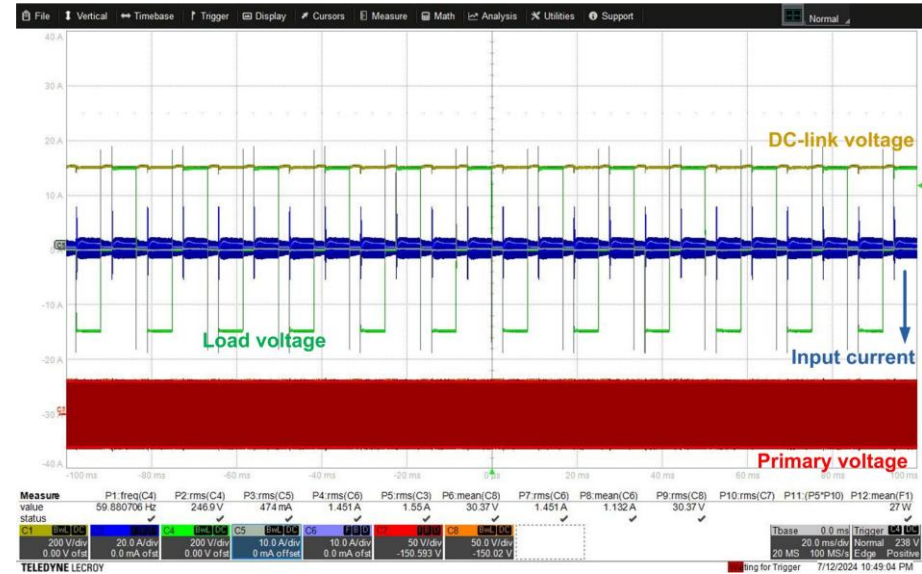- $P_{peak} \approx 30 \text{ W @ } 240V \text{ RMS}$
- $I_{load} = 1.5A$



$$V_{in} = 30V$$

- Load Voltage
- Load Current
- DC-Link Voltage
- Primary Voltage
- Input Current